 


Chapter 9.

Sequential Circuit Design Practice

Example 1: Problem Statement

- **Design 74x166 – 8 bit parallel-in, serial-out shift register with enable**



CLR – Asynchronous

EN – when asserted -> according to LD

otherwise -> hold

LD – when asserted -> LD

otherwise -> Shift

Step 1: State/Output Table

- A state table (or diagram) isn't very helpful since LD can take you from any state to any other -> messy!

– Inputs:	A-H	8	}	2^{20} rows!
	SER	1		
	CLR	1		
	EN	1		
	LD	1		
State variables:	Qs	8	}	

Alternatives

- **CLR asynchronous – not needed**
- **EN – take care in special way**
 - initially assume always asserted
- **Think 2 bits rather than 8 bits and then generalize**
- **Variables: SER, A, B, LD, Q_A , Q_B → still $2^6=64$ rows!**
→ “Variable Entered Table”

Variable-Entered Table

Q _A	Q _B	LD	Q _A	Q _B
0	0	0	SER	0
0	0	1	A	B
0	1	0	SER	0
0	1	1	A	B
1	0	0	SER	1
1	0	1	A	B
1	1	0	SER	1
1	1	1	A	B

Steps 2-6

- **Step 2: state minimization – not relevant**
- **Step 3: state assignment – not relevant**
- **Step 4: Transit/output table – we already have**
- **Step 5: Choose f/f – $D f/f$**
- **Step 6: Excitation table – same as transit table**

Steps 7-8: Excitation/Output Eqs. (Variable Entered Map)

D_A

		LD	
		0	1
$Q_A Q_B$	00	SER	A
	01	SER	A
	11	SER	A
	10	SER	A


$$D_A = \overline{LD} \cdot SER + LD \cdot A$$

D_B


		LD	
		0	1
$Q_A Q_B$	00	0	B
	01	0	B
	11	1	B
	10	1	B

$$D_B = \overline{LD} \cdot Q_A + LD \cdot B$$

Steps 9: Logic Diagram

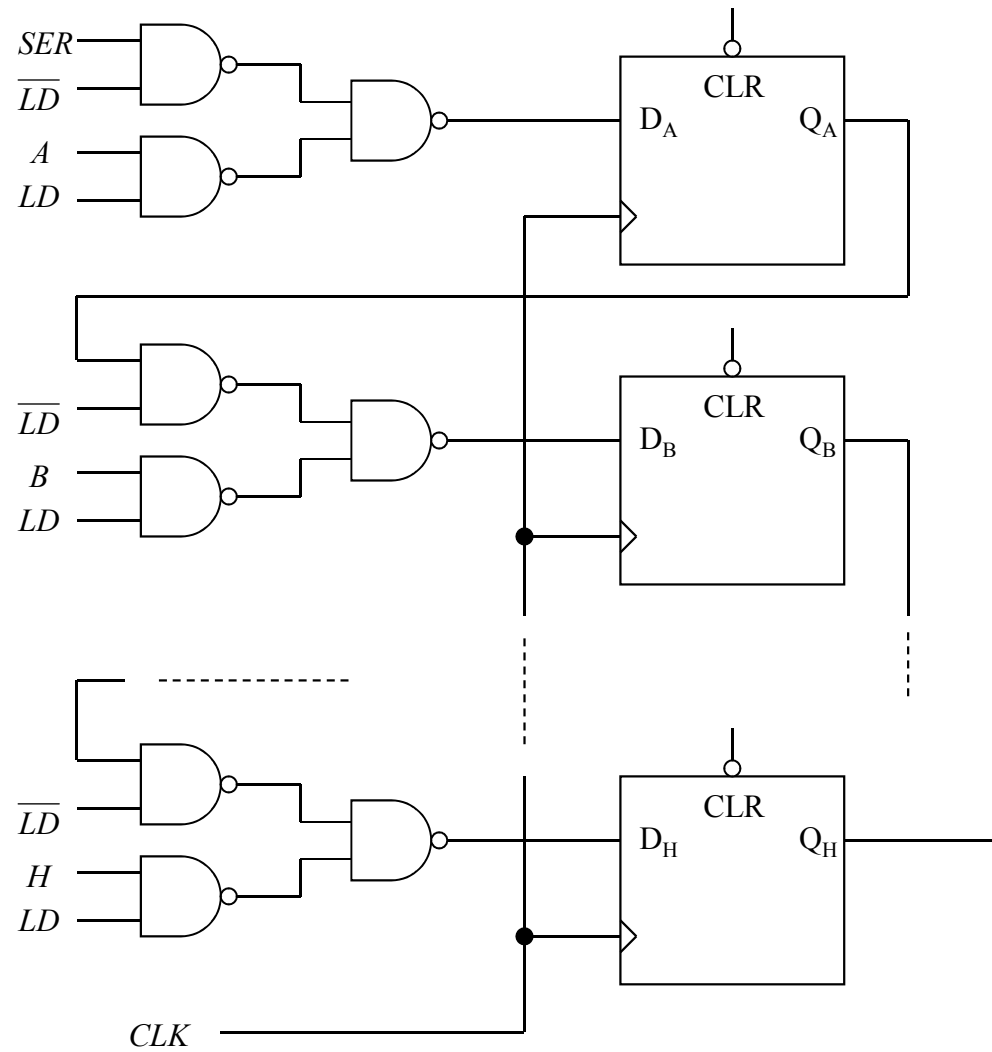


Steps 9: Logic Diagram

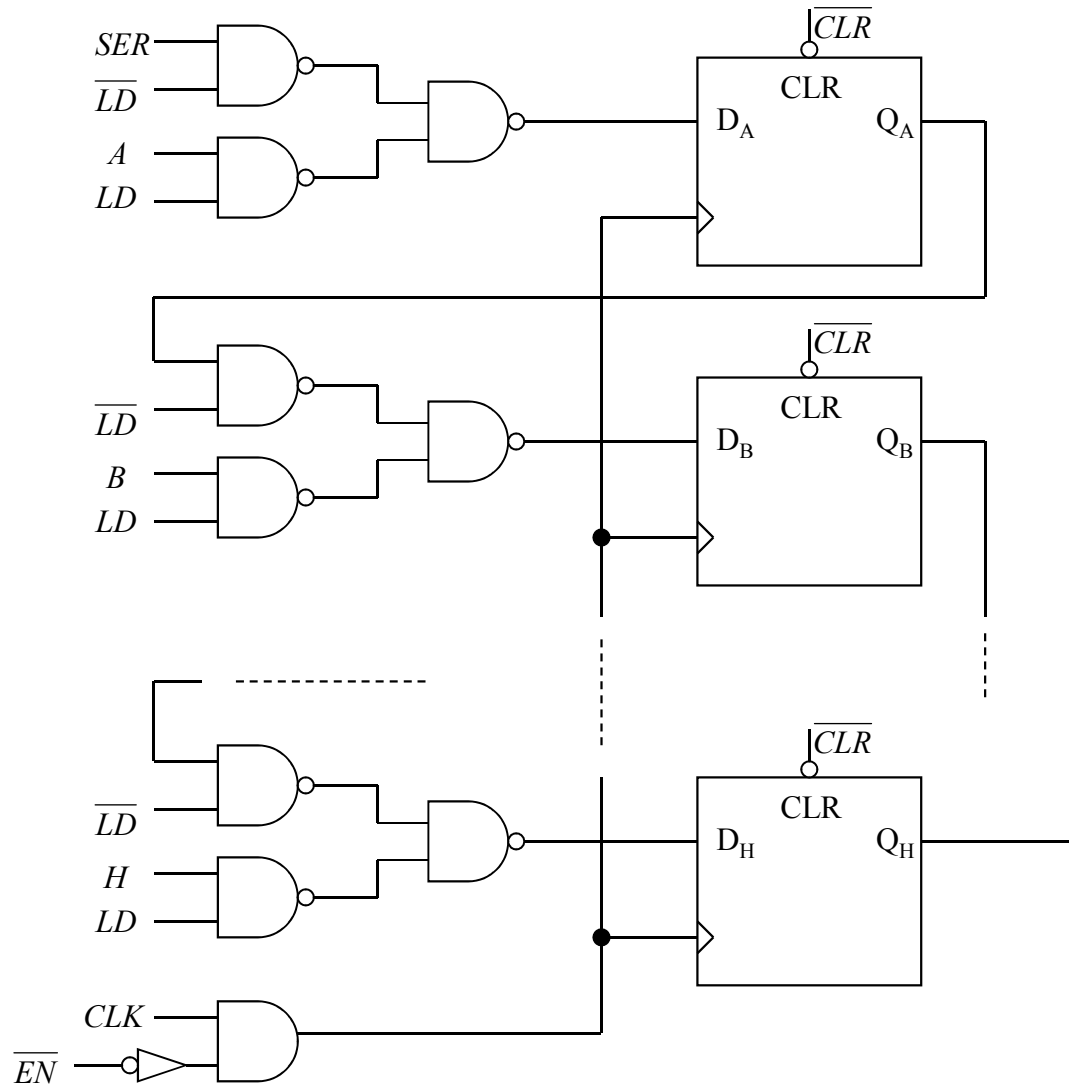


Remind

(General Sequential Circuit Structure)

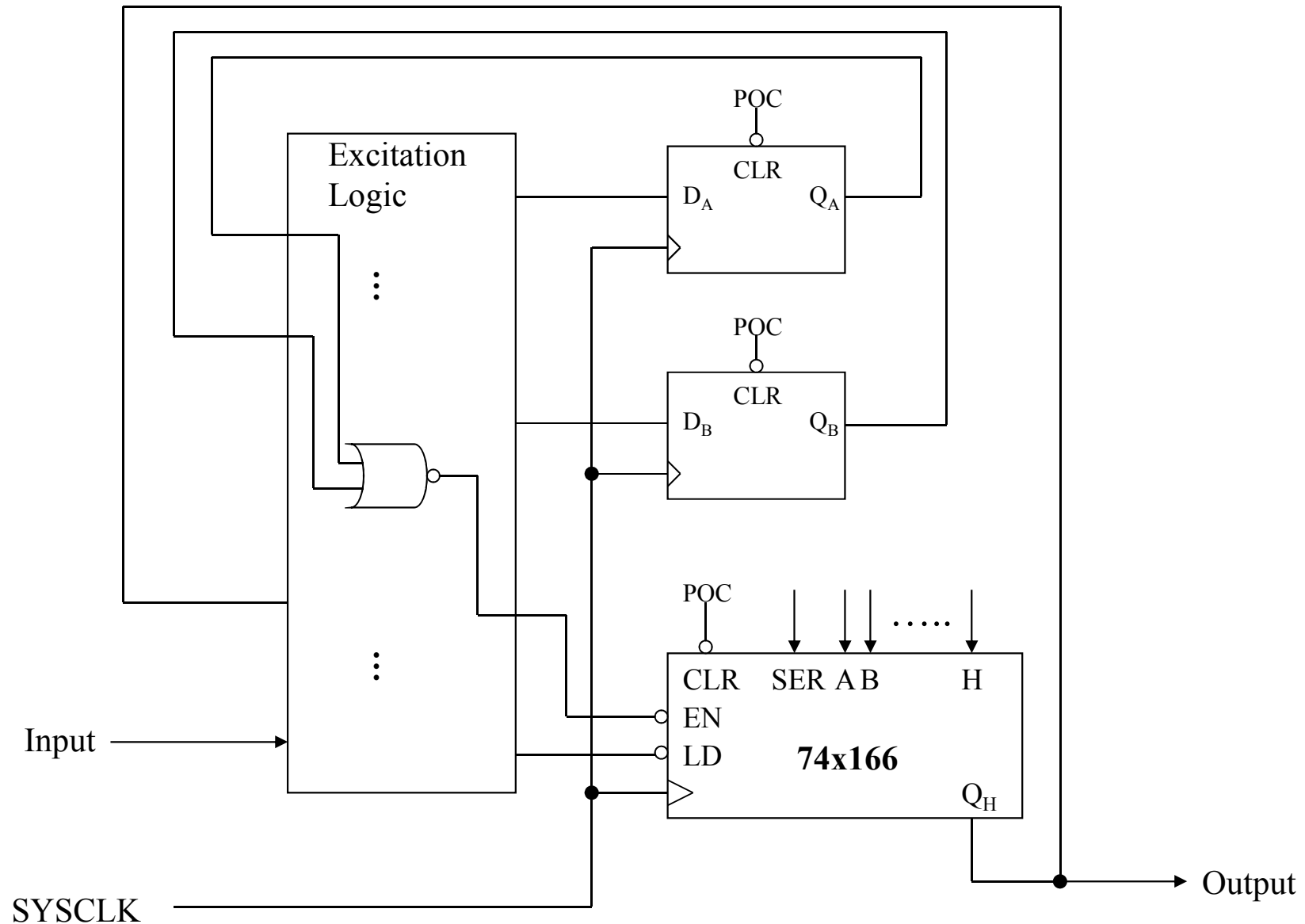


Remind

(General Sequential Circuit Structure)

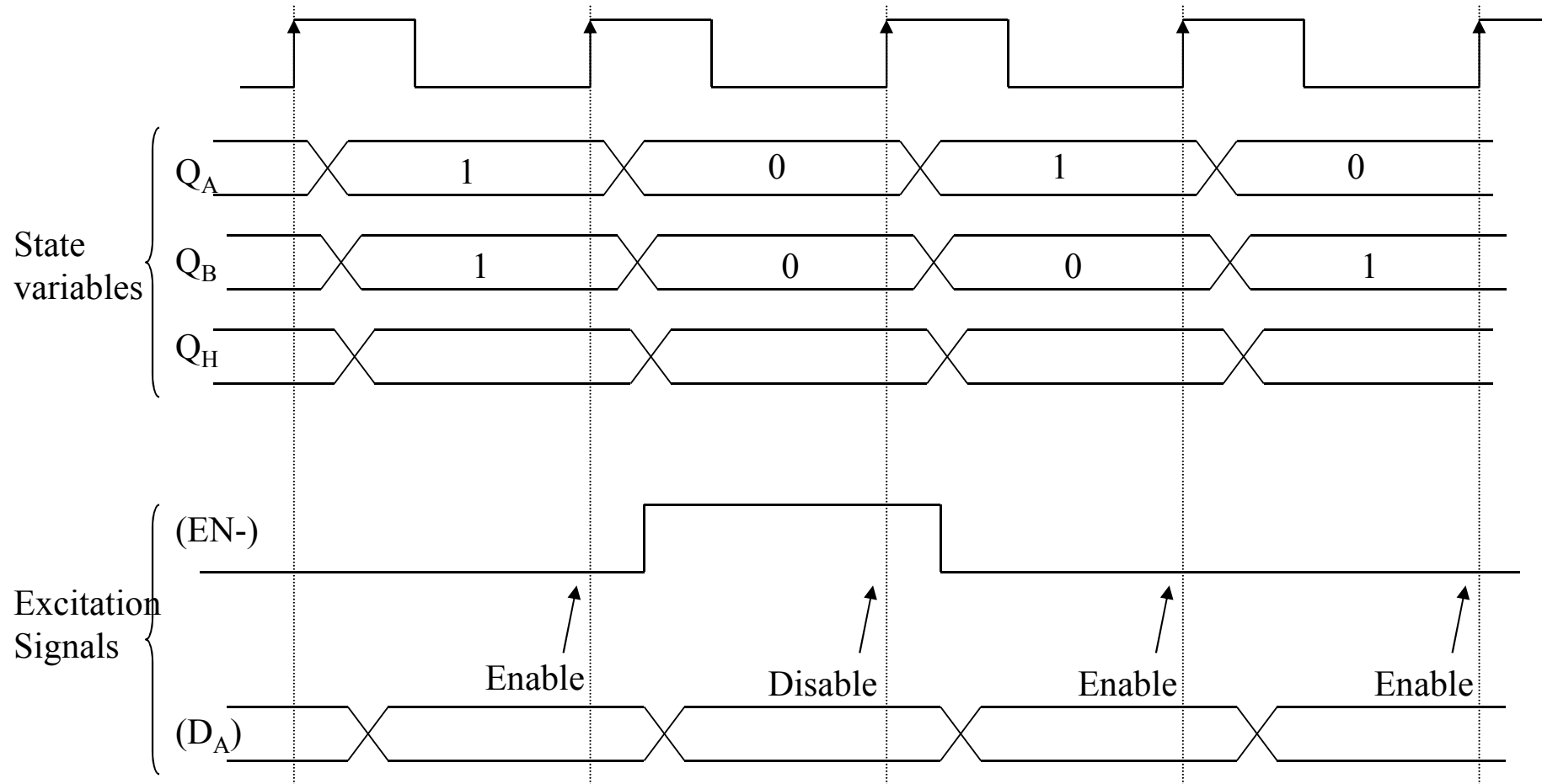

Gating the CLK

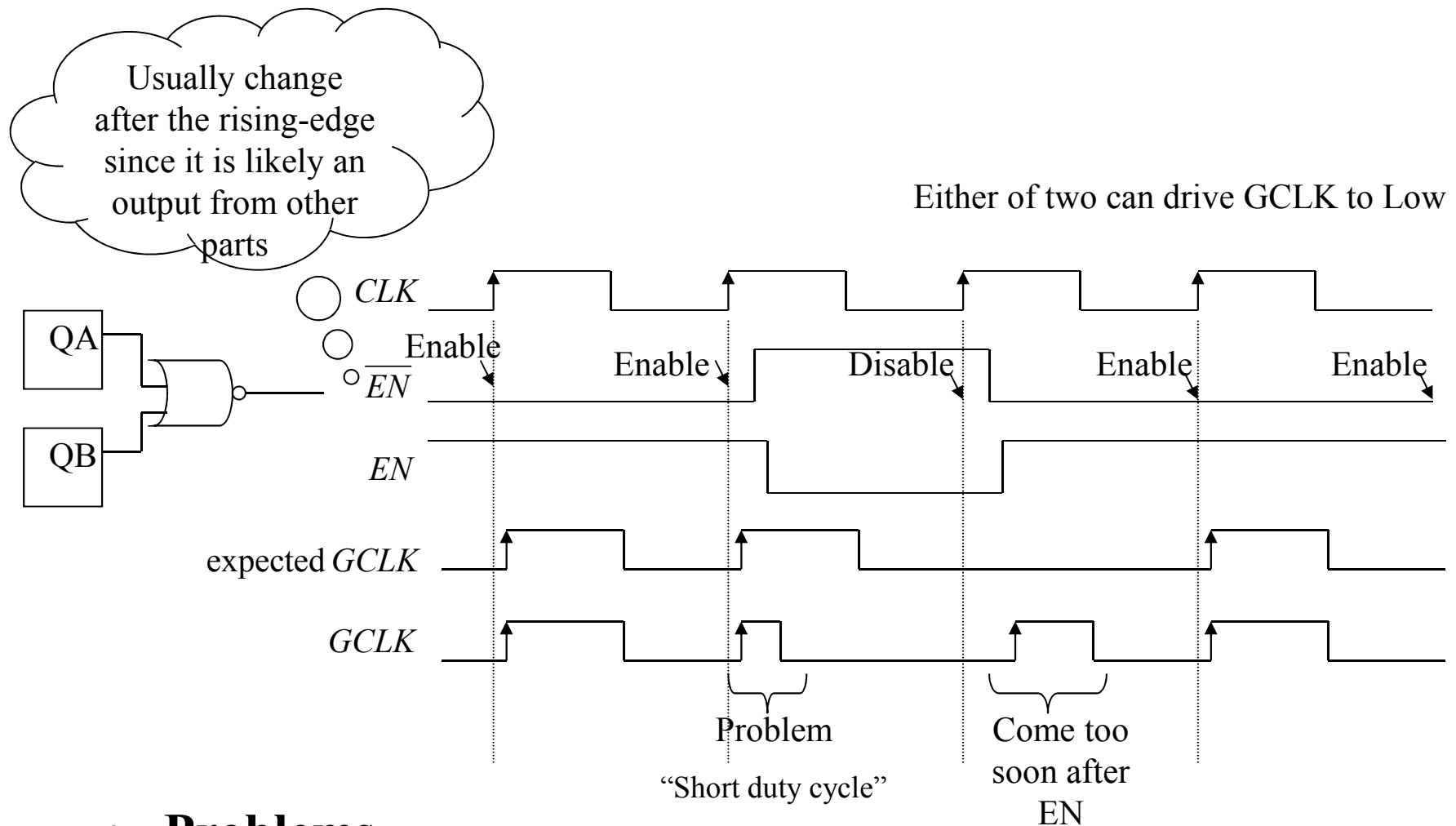


- **Problems**

- Short GCLK pulse – dependent on delay
- Comes too soon (or late) after asserting enable

Different approach to holding

 - **Delay in CLK line is not good design practice**
 - Puts in CLK skew
 - All f/f CLKs don't triggered at same time → eliminates the good points to use synchronous design (we can ignore a lot of difficult timing issues)
- **Desired: “Synchronous function-enable input”**
 - EN should sampled along with data at CLK edge





Clock Skew

- **Clock skew: difference between arrival times of CLK at different devices**
- **Caused by**
 - Gating in the CLK line
 - Delay along long lines (1ns/ft – speed of light) – CAD serial routing

Clock Skew

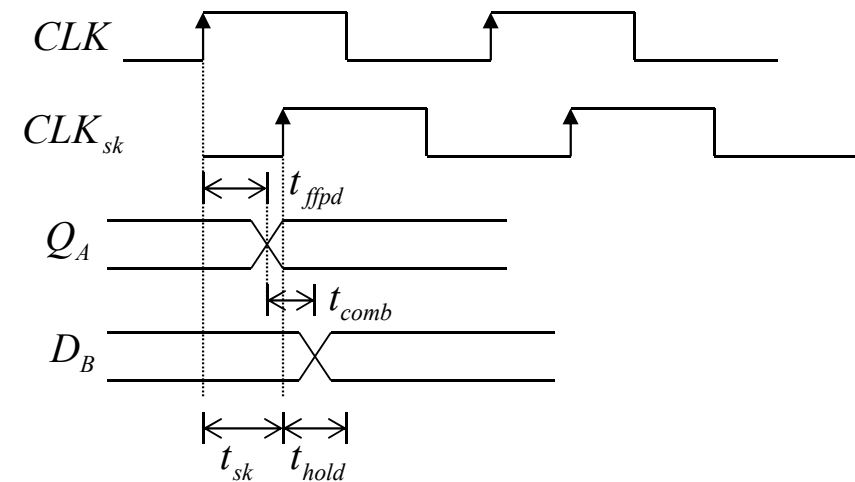 - **Problem**

- If t_{sk} too long – CLK edge get to B f/f after D_B changes \Rightarrow Wrong operations
- In general – hold time on D_B can be violated



$$t_{ffpd}(\min) + t_{comb}(\min) > t_{sk} + t_h$$

t_{sk} max?: use timing specs


$$x74(25ns) + x00(9ns) + x10(9ns) - x74hold(5ns) = 38ns$$

Example 2: Problem Statement

(Stop Watch: System Controller Approach)

- **Design a “stop watch” that can measure times taken for two events**
 - Inputs
 - CLK = 16 Hz
 - RESET: Asynchronously reset everything
 - X: comes from push button
 - First Push: Start timer
 - Second Push: Store the time taken for the first event
 - Third Push: Store the time taken for the second event
 - SEL: select output (High: first event time, Low: second event time)
 - Outputs
 - Two decimal digits to be connected to two seven segment displays
 - Can display 00 ~ 99


Overall Architecture Design

 


- Which LBB (among those we learn in the class) and how many?
- How to decompose the whole system into data part and control part?

Design System Architecture

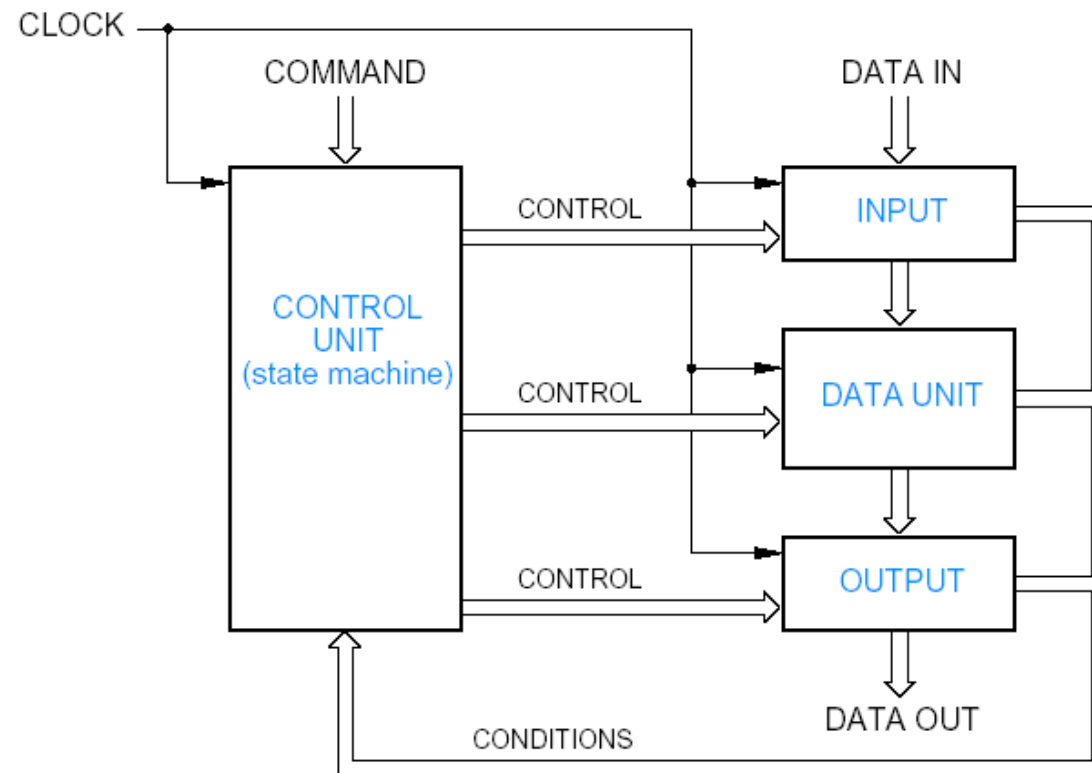- **First step: divide the system into a control unit and data unit**
 - Data unit – stores, routes, combines, and generally process data
 - Control unit – starting & stopping the process, testing conditions, and deciding what to do next



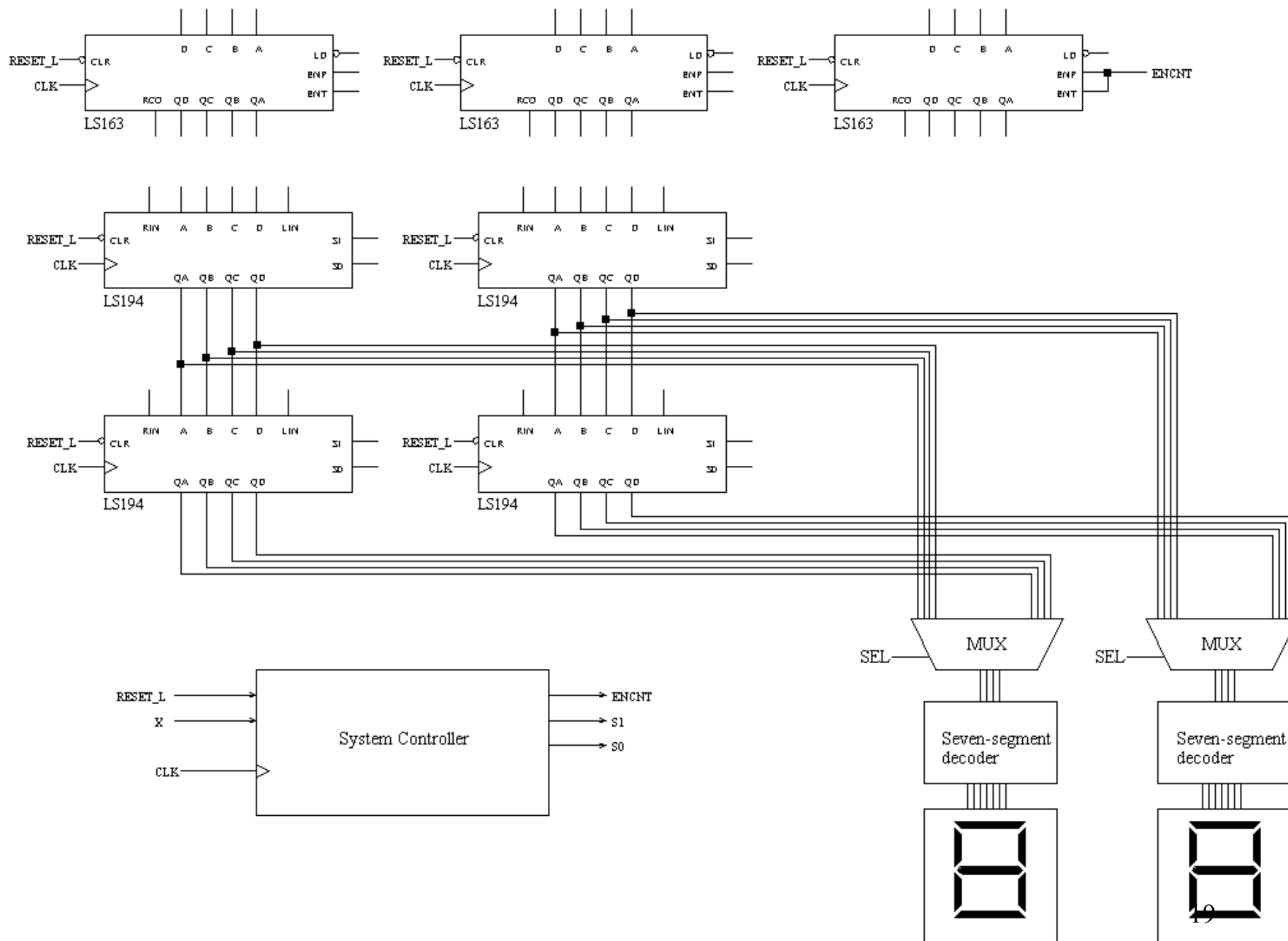

System controller design

Table (Variable Entered Table)

State symbol	P.S.	N.S.	Output
	Q1 Q0		S1 S0 ENCNT
A	0 0		
B	0 1		
C	1 1		
unused	1 0		

Excitation Eqs, Output Eqs

		Q0	
		0	1
Q1			
0			
1			

D1=

		Q0	
		0	1
Q1			
0			
1			

D0=

		Q0	
		0	1
Q1			
0			
1			

S1=

		Q0	
		0	1
Q1			
0			
1			

S0=

		Q0	
		0	1
Q1			
0			
1			

ENCNT=

Alternative (Verilog program)

ISE Project Navigator (P49d) - D:\Documents\Xilinx\stopWatch\stopWatch.xise - [syscontrol.v]

File Edit View Project Source Process Tools Window Layout Help

Design View: Implementation Simulation

Hierarchy

- stopWatch
 - xc3s500an-4tgg144
 - data.v
 - syscontrol (syscontrol.v)

No Processes Running

Processes: syscontrol

- Design Summary/Reports
- Design Utilities
 - Create Schematic Symbol
 - View Command Line Log File
 - View HDL Instantiation Template...
- User Constraints
- Synthesize - XST
 - View RTL Schematic
 - View Technology Schematic
 - Check Syntax
 - Generate Post-Synthesis Simulation
- Implement Design
 - Generate Programming File
 - Configure Target Device
 - Analyze Design Using ChipScope

```

1 `timescale 1ns / 1ps
2
3 module syscontrol(CLK, RESET_L, X, ENCNT, S1, S0);
4   input CLK;
5   input RESET_L;
6   input X;
7   output reg ENCNT;
8   output S1, S0;
9   parameter Stop = 2'b00,
10              Wait1st = 2'b01,
11              Wait2nd = 2'b10;
12   reg [1:0] Sreg;
13   wire RESET;
14
15   assign RESET = ~RESET_L;
16
17   /* state machine */
18   always @(posedge CLK) begin
19     if(RESET) Sreg <= S0;
20     else begin
21       case (Sreg)
22         Stop : if(X==0) Sreg <= Stop;
23              else Sreg <= Wait1st;
24         Wait1st : if(X==0) Sreg <= Wait1st;
25                 else Sreg <= Wait2nd;
26         Wait2nd : if(X==0) Sreg <= Wait2nd;
27                 else Sreg <= Stop;
28         default : Sreg <= Stop;
29       endcase
30     end
31   end

```

Design Summary (Synthesized) syscontrol.v

Console

```

=====
*                               *
=====
Clock Information:
-----
No clock signals found in this design

Asynchronous Control Signals Information:
-----
No asynchronous control signals found in this design

Timing Summary:
-----
Speed Grade: -4


Minimum period: No path found
Minimum input arrival time before clock: No path found
Maximum output required time after clock: No path found
Maximum combinational path delay: No path found
=====

Process "Synthesize - XST" completed successfully

```

Find in Files Results Warnings Errors Console

Ln 23 Col 46 Verilog

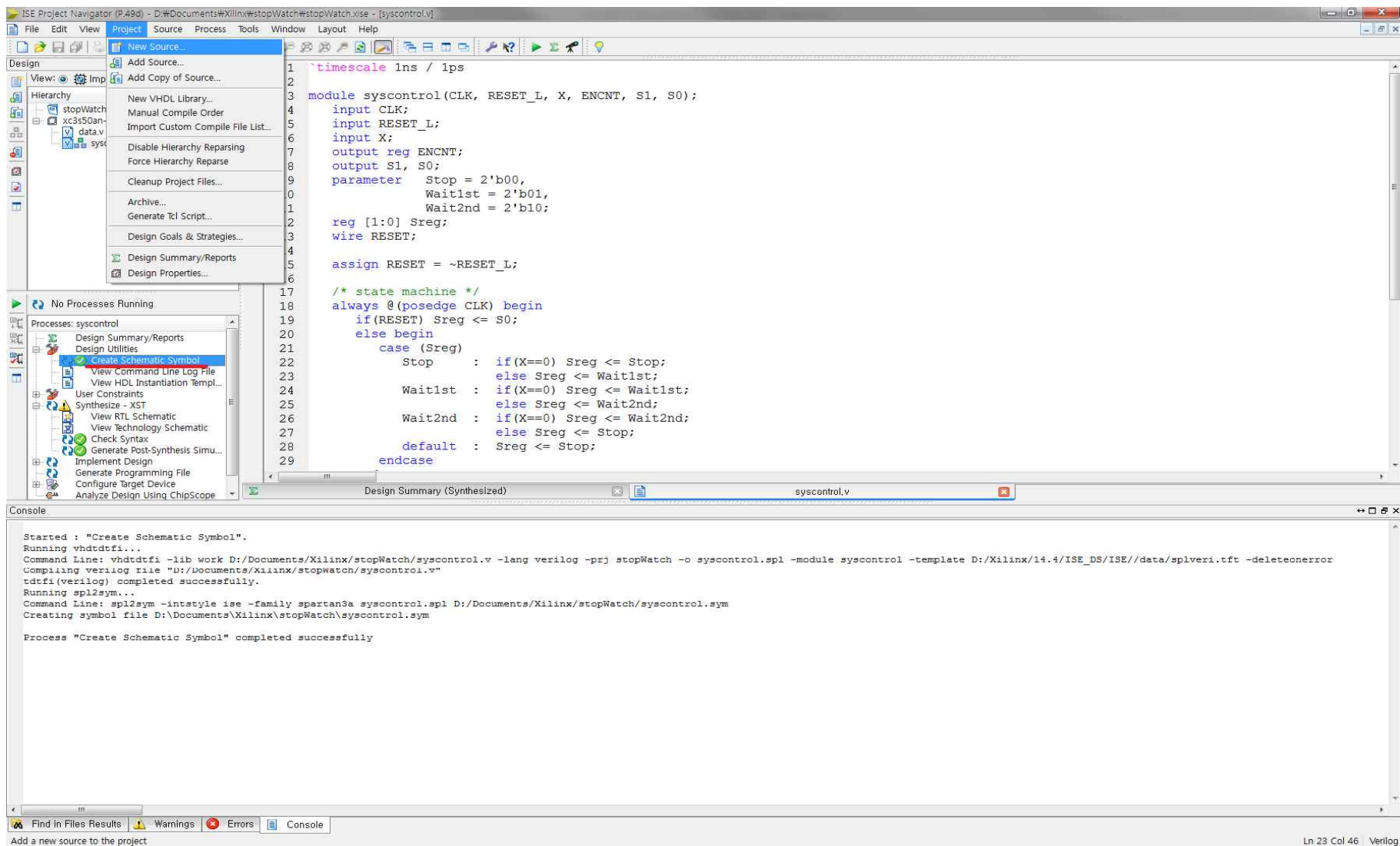

ISE Project Navigator (P49d) - D:\Documents\Xilinx\stopWatch\stopWatch.xise - [D:\Documents\Xilinx\stopWatch\total.sch]

File Edit View Project Source Process Add Tools Window Layout Help

Symbols

Categories

- <<-All Symbols-->
- <D:\Documents\Xilinx\stopWat...
- Advanced
- Arithmetic
- Buffer
- Carry_Logic
- Clocking_Resources
- Comparator
- Counter
- Decoder
- Flip_Flop
- General
- IO

Symbols

- data
- syscontrol

Symbol Name Filter

Orientation

Rotate 0

Symbol Info

Libraries Symbols Options

Design Summary (out of date)

D:\Documents\Xilinx\stopWatch\total.sch

data.v

Console

```

Started : "Create Schematic Symbol".
Running vhdtdtfi...
Command Line: vhdtdtfi -lib work D:/Documents/Xilinx/stopWatch/data.v -lang verilog -prj stopWatch -o data.spl -module data -template D:/Xilinx/14.4/ISE_DS/ISE//data/splveri.tft -deleteonerror
Compiling verilog file "D:/Documents/Xilinx/stopWatch/data.v"
tdtfi(verilog) completed successfully.
Running spl2sym...
Command Line: spl2sym -intstyle ise -family artix7 data.spl D:/Documents/Xilinx/stopWatch/data.sym
Creating symbol file D:\Documents\Xilinx\stopWatch\data.sym


Process "Create Schematic Symbol" completed successfully


Started : "Launching Schematic Editor to edit total.sch".

```

Delete the selection

[836,628]

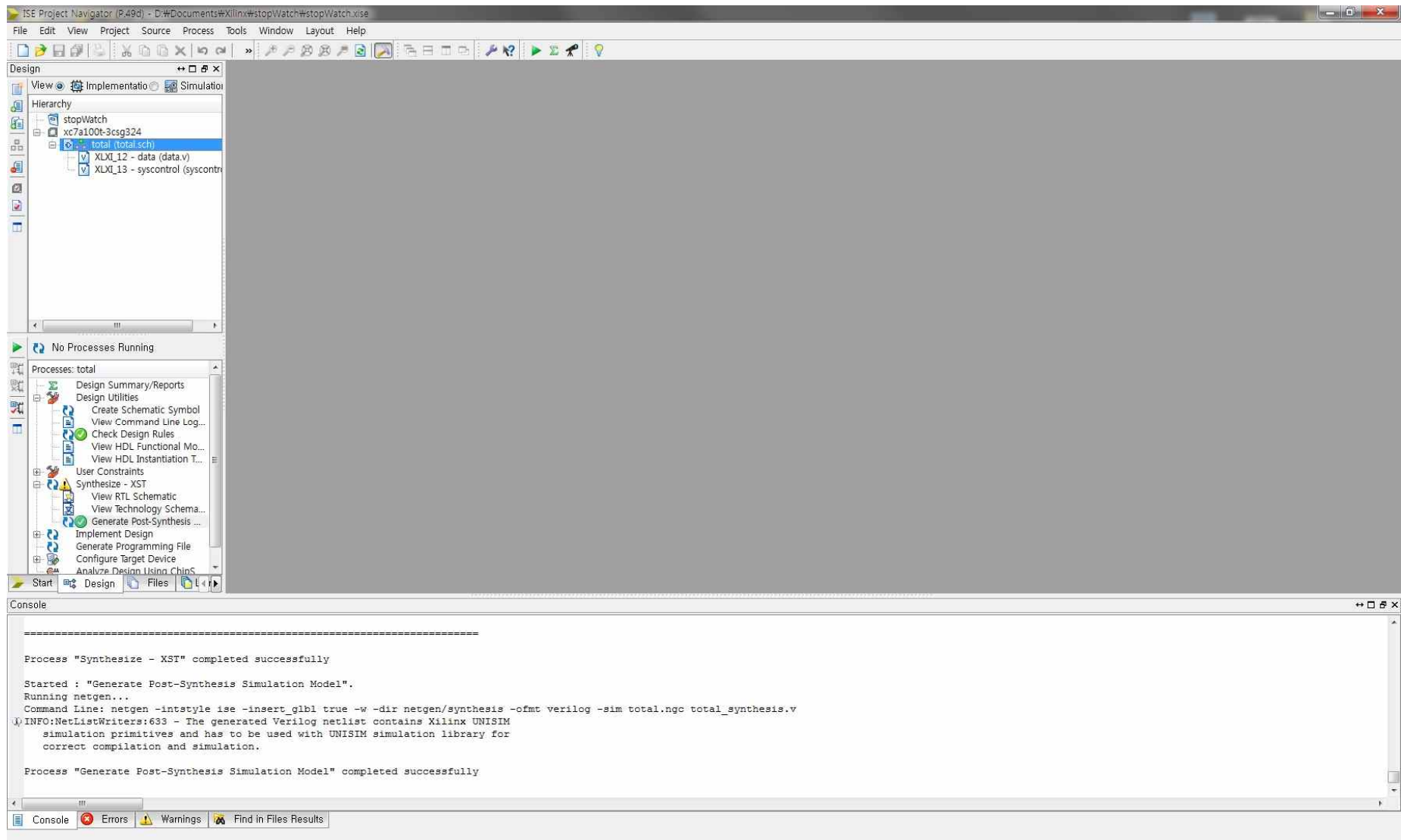

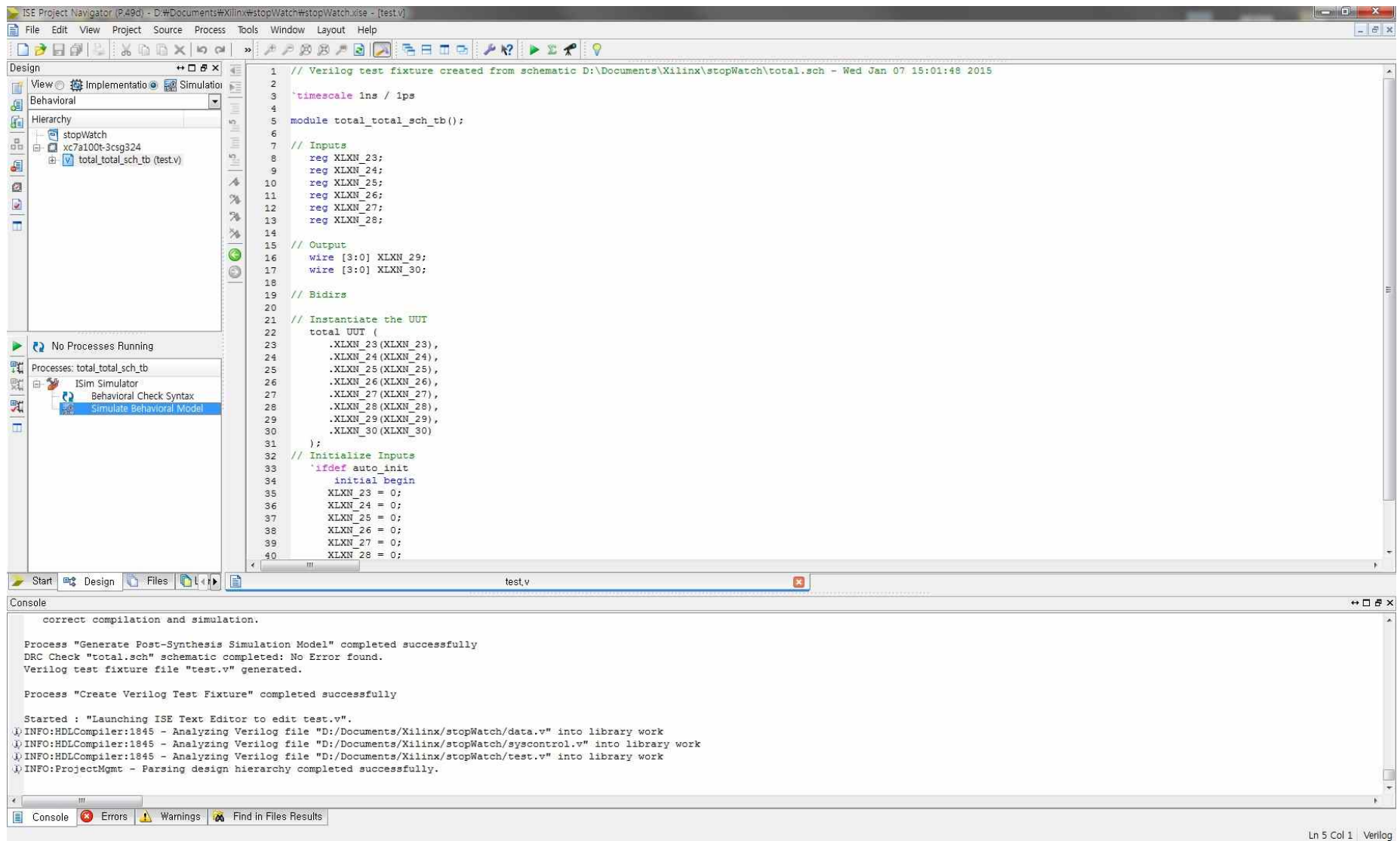


Example 3: 4-bit Serial Adder

(Decomposing state machines, synchronous design methodology, system controller design)


Review of combinational adders

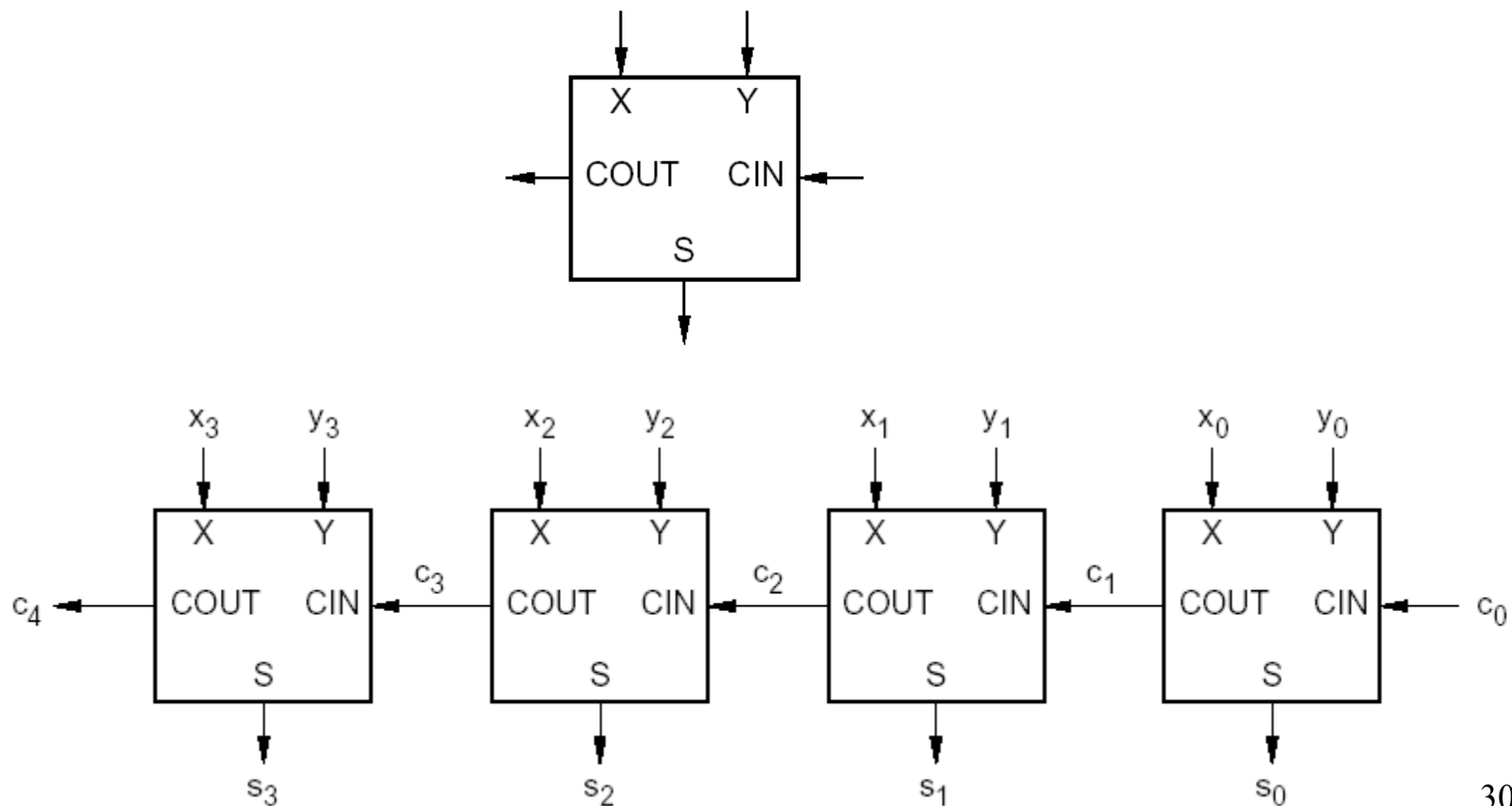- 1-bit full adder and 4-bit ripple adder



Binary serial adder

 - **Serial input feed (two data streams A and B)**
- **Generate serial output**





CLR – clear the previous carry synchronously

HOLD – hold the previous value of the carry

Binary serial adder implementation


- LS183: dual 1 bit full adders

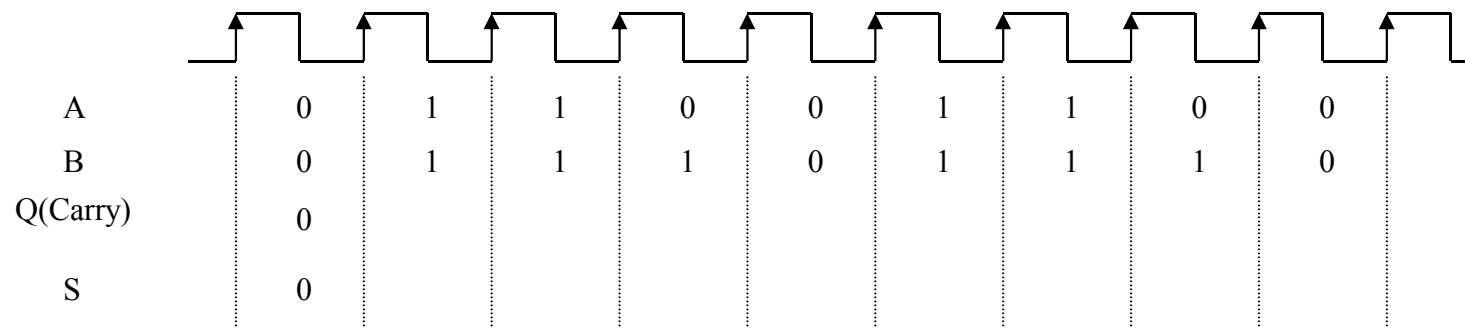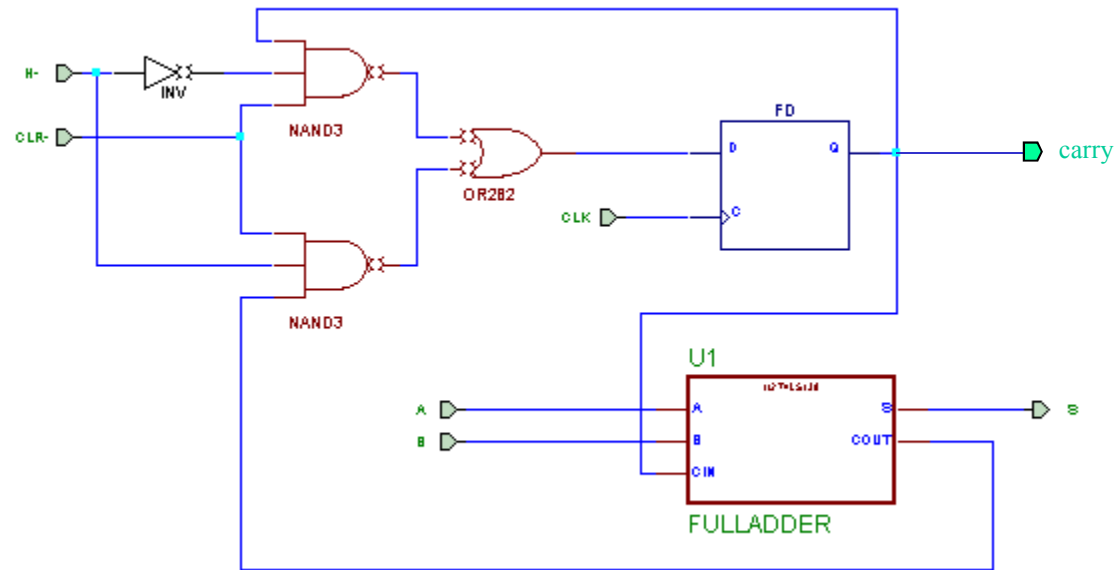

 Problem Statement

- **Design a 4-bit adder based on a serial approach**

- Parallel feed of X_1 and X_2
- Parallel out of Y comes out after few cycles
- Final carry available




Start from LBB


- **Here, we have some basic building blocks in mind**
 - 4-bit shift registers, binary serial adder, etc
- **Tie these elements together and make them controllable from the outside world**
- **We want to take maximum advantage of common building blocks (MSI chips that are available)**

Design System Architecture

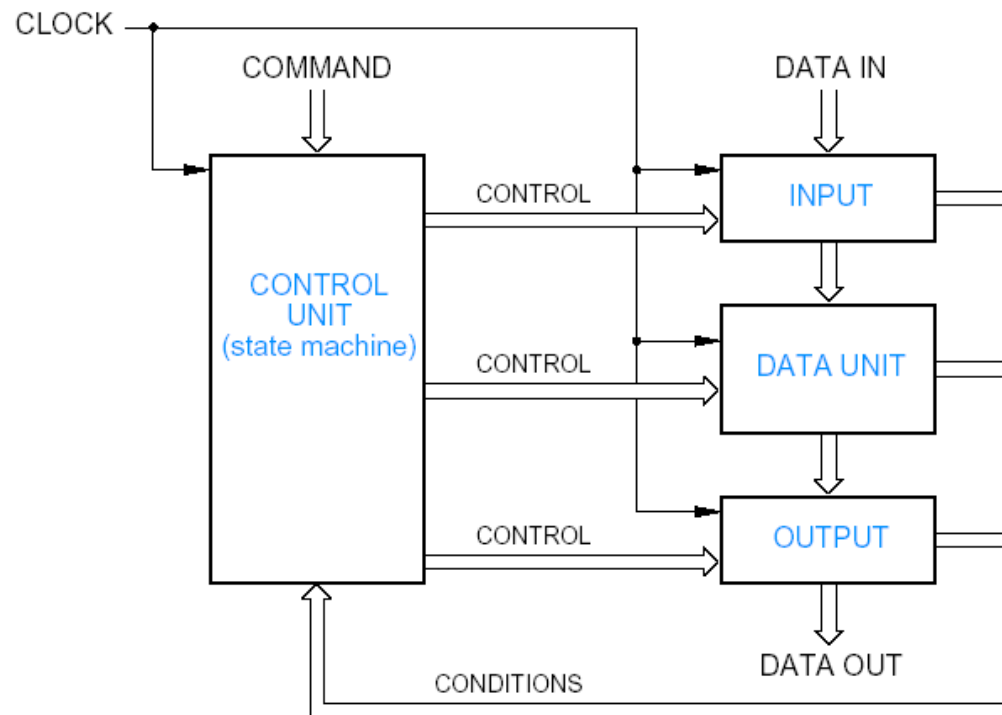
- **First step: divide the system into a control unit and data unit**
 - Data unit – stores, routes, combines, and generally process data
 - Control unit – starting & stopping the process, testing conditions, and deciding what to do next



Data unit & Control unit

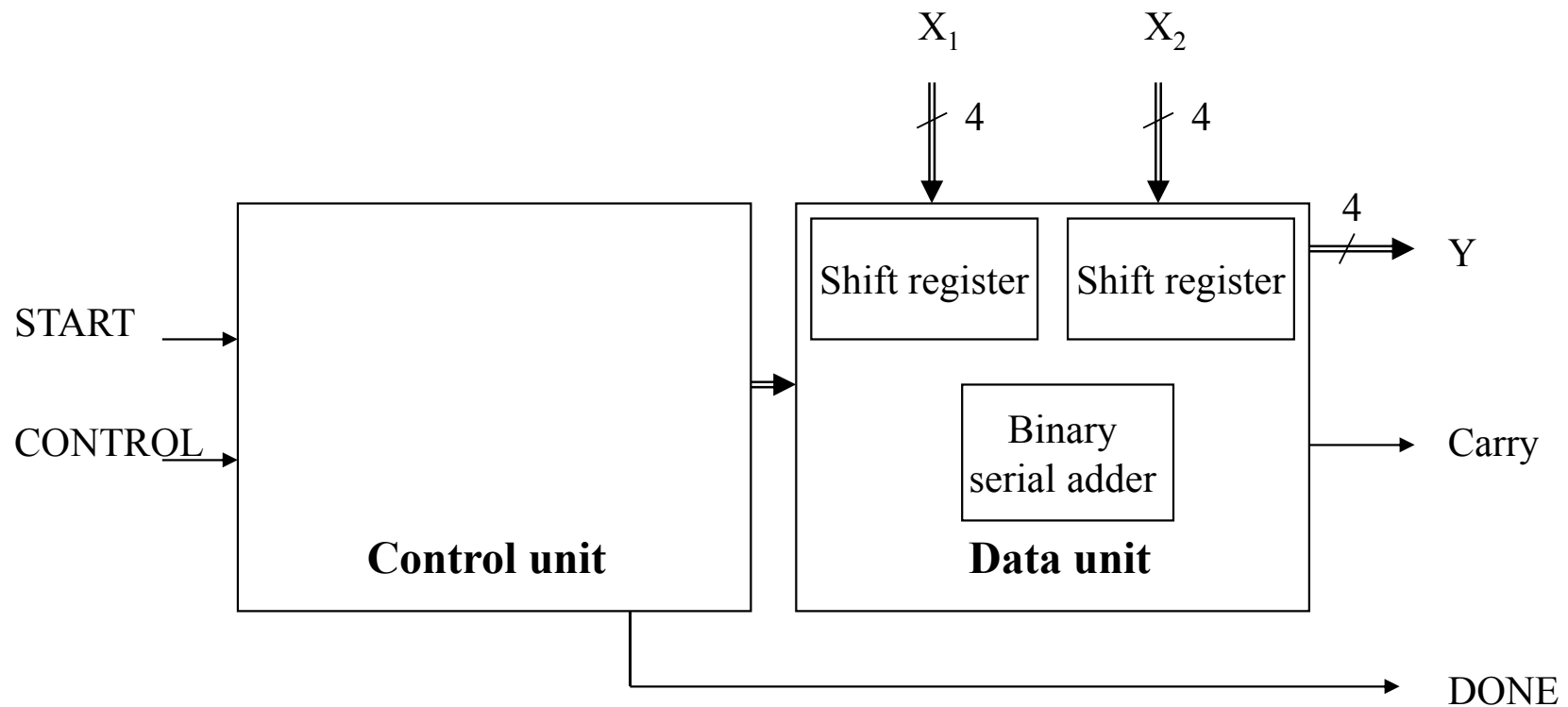


Architecture

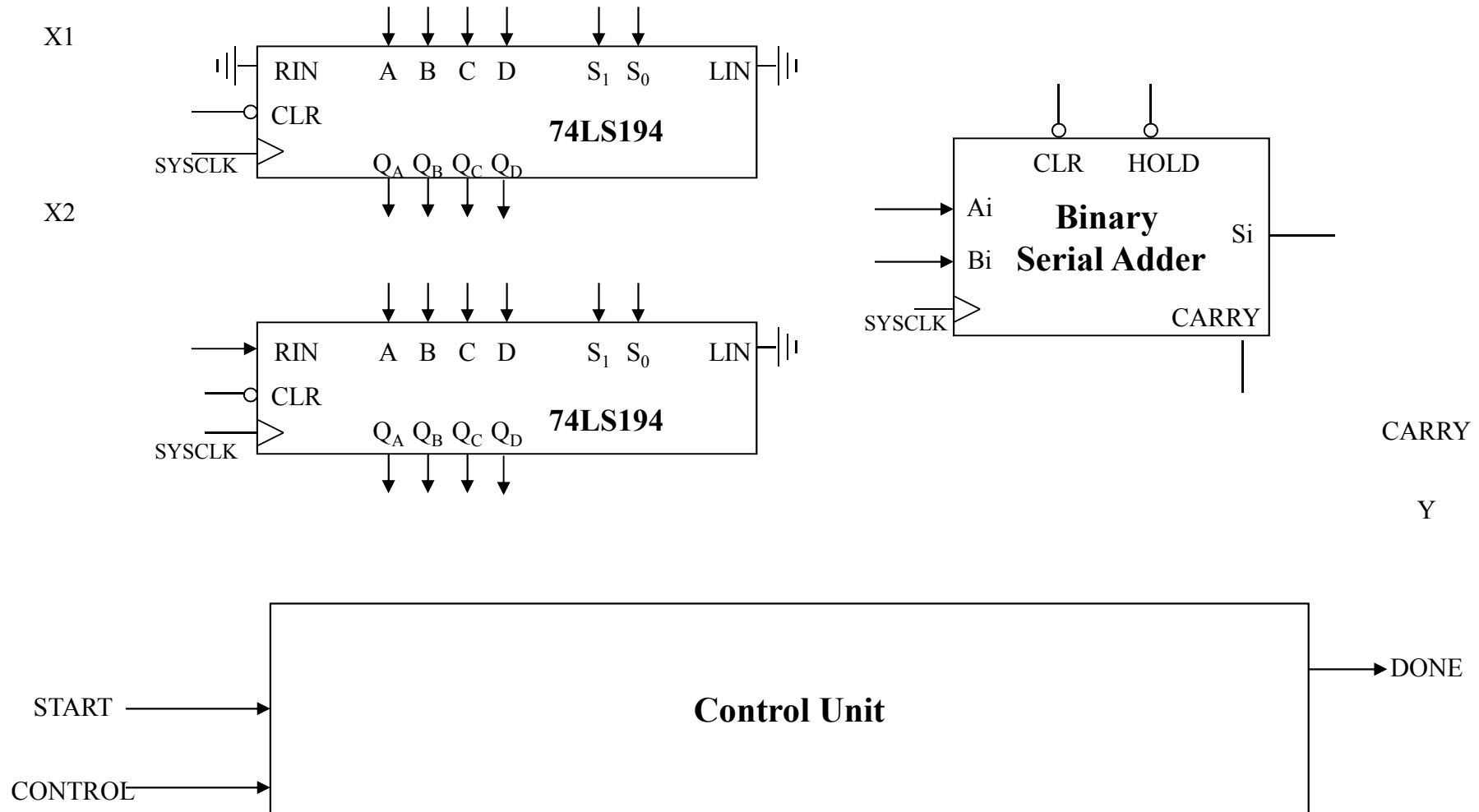


Decomposing state machine

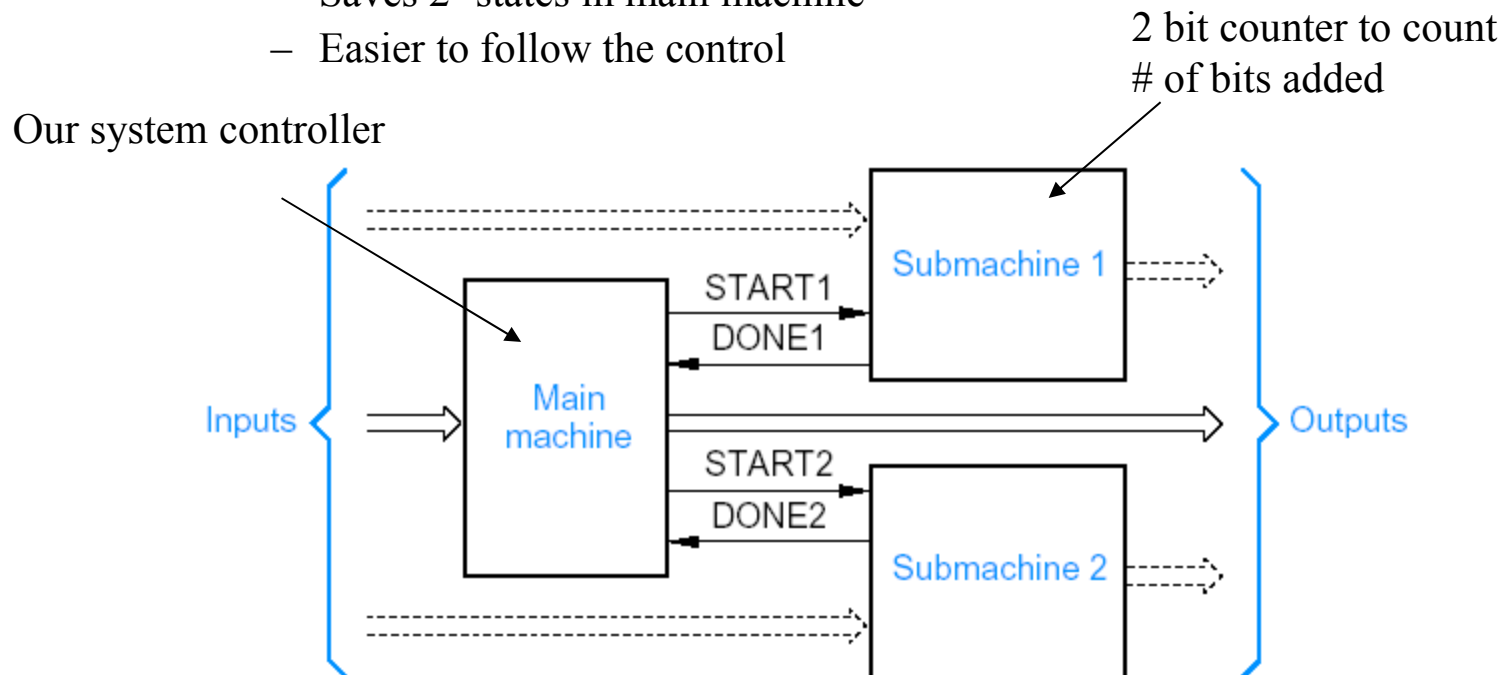
- **Second step: the state machine part (control unit) can be decomposed into several parts**
 - Main machine (system controller) – provides the primary inputs and outputs and does top level control
 - Submachines – perform lower-level steps under control of main machine
 - Typical submachine – counter
 - Saves 2^n states in main machine
 - Easier to follow the control



Architecture

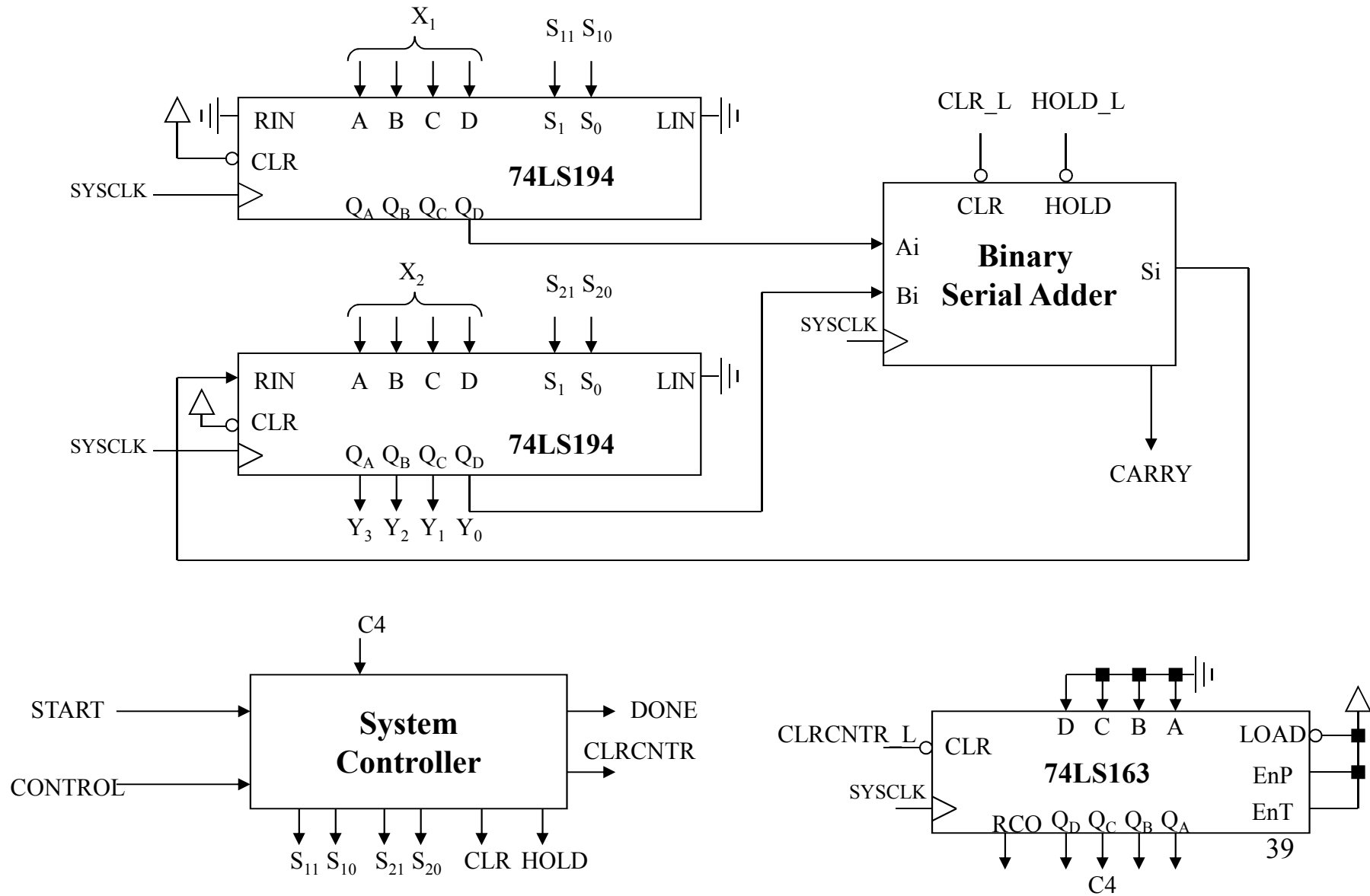

System controller design

 

Example results

0101 (5)					
+ 0001 (1)					

0110 (6)					
	Sate	Carry	Reg 1	Reg 2	Counter
a	-	-	-	-	0
b	-	-	-	-	0
c	0	0101	0001		1
c	1	0010	0000		2
c	0	0001	1000		3
c	0	0000	1100		4
d	0	0000	0110		5

State assignment and Transition Table

	Q1Q0	Q1Q0 (D1D0)	DONE	CLRCNTR	CLR	HOLD	S11	S10	S21	S20
a	0 0	0 ST	1	1	0	1	x	x	0	0
b	0 1	1 1	0	0	1	x	1	1	CONT	CONT
c	1 1	1 $\overline{C4}$	0	0	0	0	0	1	0	1
d	1 0	ST 0	1	x	0	1	x	x	0	0

Excitation and Output Eqs.

		Q ₀	
		0	1
Q ₁	0	0	1
	1	ST	1

$$D_1 = Q_0 + ST \cdot Q_1$$

		0	1
	0	ST	1
	1	0	$\overline{C4}$

$$D_0 = \overline{Q_1}Q_0 + \overline{Q_1} \cdot ST + Q_0 \cdot \overline{C4}$$

		Q ₀	
		0	1
Q ₁	0	1	0
	1	1	0

$$DONE = \overline{Q_0}$$

		Q ₀	
		0	1
Q ₁	0	1	0
	1	x	0

$$CLRCNTR = \overline{Q_0}$$

		Q ₀	
		0	1
Q ₁	0	0	1
	1	0	0

$$CLR = \overline{Q_1}Q_0$$

		Q ₀	
		0	1
Q ₁	0	1	x
	1	1	0

$$HOLD = \overline{Q_0}$$

		Q ₀	
		0	1
Q ₁	0	x	1
	1	x	0

$$S_{11} = \overline{Q_1}$$

		Q ₀	
		0	1
Q ₁	0	x	1
	1	x	1

$$S_{10} = 1$$

		Q ₀	
		0	1
Q ₁	0	0	c
	1	0	0

$$S_{21} = \overline{Q_1}Q_0 \cdot CONTROL$$

		Q ₀	
		0	1
Q ₁	0	0	c
	1	0	1

$$S_{20} = Q_0 \cdot CONTROL + Q_1Q_0$$


Logic Diagram

Asynchronous Inputs and Output Glitches

- **Things to watch out for in synchronous design**
 - Clock skew
 - Gating the clock
 - Asynchronous inputs
 - Output glitches

 Example

- **Binary counting order for our previous state assignment**



	Q1Q0	Q1Q0 (D1D0)	DONE	CLRCNTR	CLR	HOLD	S11	S10	S21	S20
a	0 0	0 ST	1	1	0	1	x	x	0	0
b	0 1	1 0	0	0	1	x	1	1	CONT'	CONT'
c	1 0	1 C4	0	0	0	0	0	1	0	1
d	1 1	ST ST	1	x	0	1	x	x	0	0

Focus on part of solution

$Q_1 \backslash Q_0$	0	1
0	0	1
1	1	ST

	0	1
0	ST	0
1	C4	ST

$Q_1 \backslash Q_0$	0	1
0	1	0
1	0	1


$Q_1 \backslash Q_0$	0	1
0	-	1
1	0	-

$$D_1 = Q_1 \overline{Q_0} + \overline{Q_1} Q_0 + ST \cdot Q_1$$


$$D_0 = ST \cdot \overline{Q_1} \overline{Q_0} + ST \cdot Q_1 Q_0 + C4 \cdot Q_1 \overline{Q_0}$$

$$DONE = \overline{Q_1} \overline{Q_0} + Q_1 Q_0$$


$$S11 = Q_0$$

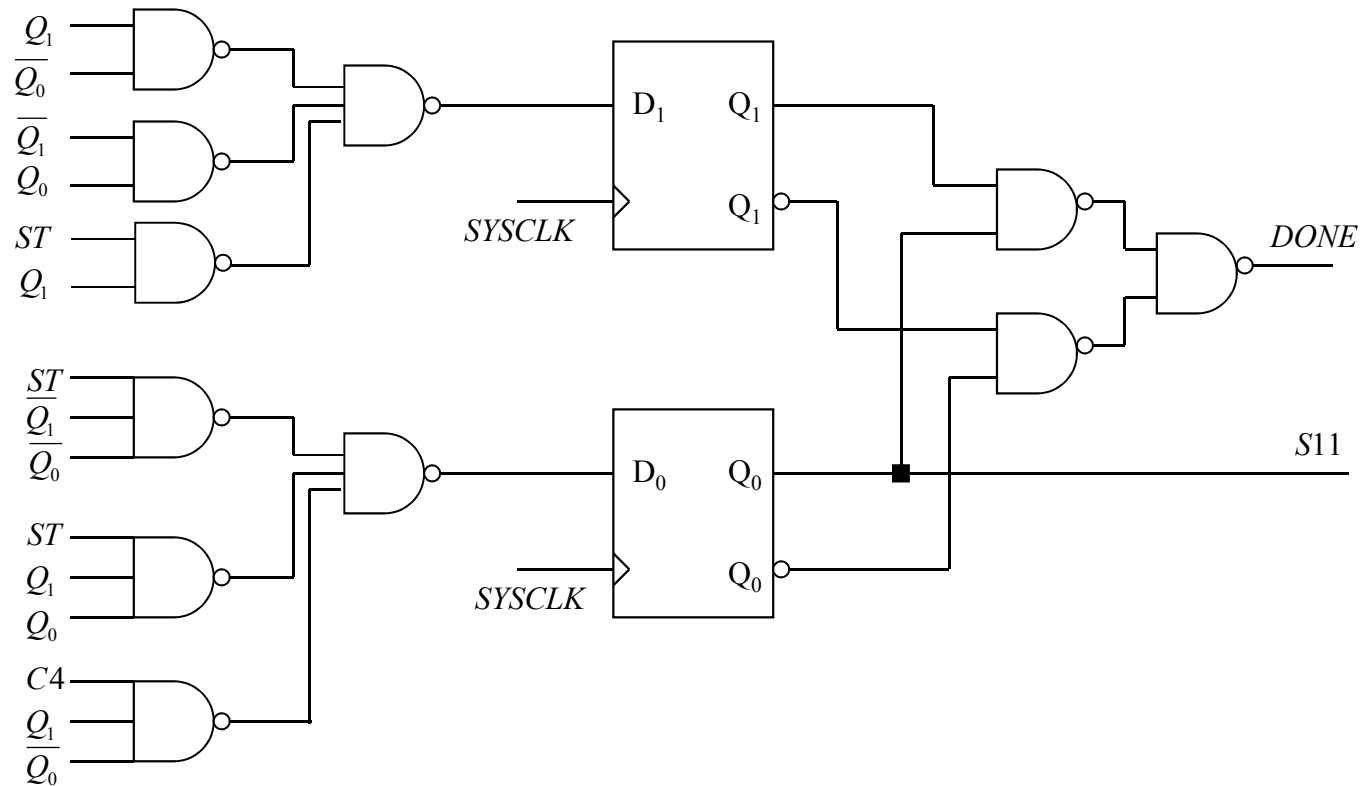

Asynchronous START

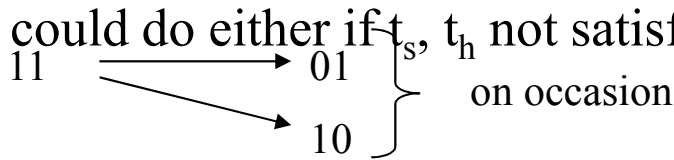- **Is START synchronous or asynchronous?**
 - Could be either
 - Assume asynchronous (comes from another system not using same SYSCLK)
- **Look at transition from “11” to “00” by negating START**
- **What happens if t_s , t_h of D f/fs are not satisfied due to asynchronous START?**
 - Usually stay at 1 or go to 0
 - Problem? – early change to START=0 \Rightarrow “00”
late change to START=0 \Rightarrow “11”
- **Problem: unexpected results can happen**
 - Delays not equal, f/fs different
 - Generally – could do either if t_s , t_h not satisfied on occasion
 

Synchronize START (Synchronizer)

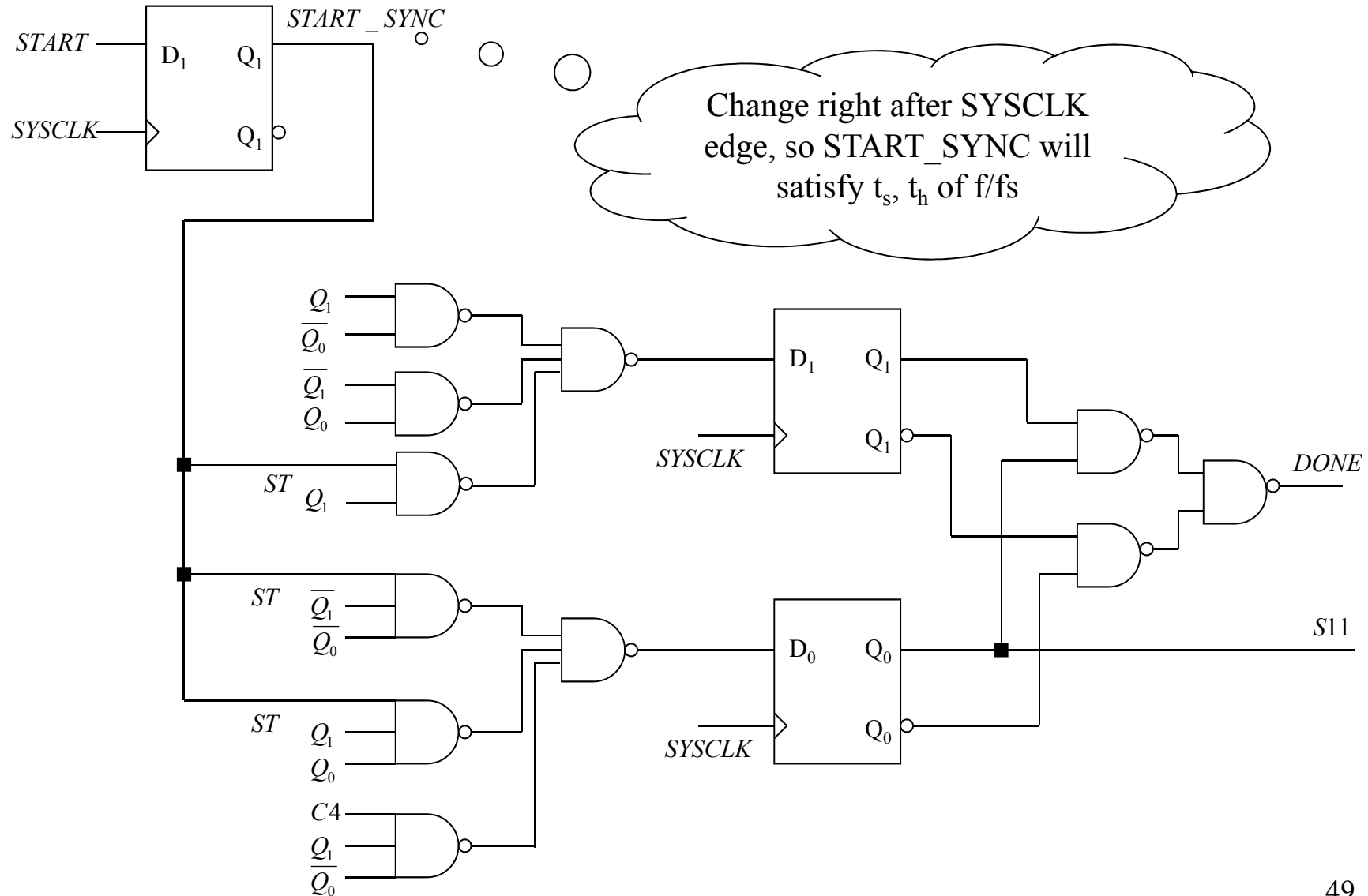


Additional Problem?

- **What else besides START_SYNC=1 or 0?**
- **Metastable – stuck in middle for a while**
 - What happen if START does not satisfy t_s , t_h of “Synchronizer” D f/f
 - START_SYNC not 1 or not 0 for a while
- **Metastability – real problem** (early versions of several microprocessor chips had this problem!)
- **Synchronizer Failure and Metastability**
 - Solutions?


Output Glitch on DONE

 - Look at transition between b="01" and c="10"



One f/f change at a time because slightly different delays

 - For a moment in the transition from "01" to "10"
 - $Q_1Q_0 = "00"$ or $"11"$
 - DONE=1 between states b ("01") and c ("10")




Problem? May or may not.
DONE is used for synchronous inputs of other parts – not likely the problem
What if DONE is used for asynchronous CLR of other parts?

- **One D f/f on DONE**



Work?

 - **DONE_REG delayed – usually no problem**



- **Register output not always needed**
 - Good state assignment (compare this with our first state assignment)
 - Some good output logics (e.g., S11)

Synchronous Design Methodology (Summary)

- **All LBBs and f/fs are clocked by the same common clock signal**
 - We use guaranteed LBBs and f/fs by the manufacturer (critical race free!!)
 - Glitches on combinational circuits connecting LBBs and f/fs have no effect, since the control inputs are sampled only after the glitches have had a chance to settle out
- **Three tasks to ensure reliable system operation**
 - Minimize and determine the amount of clock skew
 - Ensure that f/fs have positive setup- and hold-time margins
 - Identifying asynchronous inputs, synchronize them with the clock
 - Filter any problematic output glitches with output stabilizers