
 


Logic design, mid-term, Oct. 31, 2012. 11am-noon

 1. How can you express Z_1 in a Boolean expression of inputs X and Y ? Here, 3V is high voltage (TRUE) and 0V is low voltage (FALSE). (10p)



2. Represent output F in terms of Boolean expression. Then check whether F is equivalent to a certain logic gate of two inputs X and Y . (15p)



3. Use a Boolean cube to minimize the function $F(A,B,C) = \sum m(3,5,6,7)$. (15p)

4. Explain function1 in the Verilog code below. (15p)

```
module function1 (out, a, b);  
    input        a, b;  
    output       out;  
    reg          out;  
    always @(a or b) begin  
        #6 out = a ^ b;  
    end  
endmodule
```

5. $F(A,B,C) = \sum m(0,2,6,7)$. Implement function F by using 4:1 MUX. Also, draw the internal logic of 4:1 MUX. (20p)

6. Design a 4-bit adder/subtractor system that carries out $A+B$ and $A-B$. For instance, the 4 bits of B are denoted by B_3, B_2, B_1 , and B_0 , where B_3 is MSB and B_0 is LSB. Use modules of 1-bit full adders and 2:1 MUXs. That is, the internal logic of a full adder and a MUX need not be drawn. Note that 2s complement is used for $-B$. Inputs are 4 bits of A, B, B' , Control bit (0: ADD, 1: SUBTRACT). Outputs are 4 bits of S (sum) and Overflow bit. (25p)